



Project report on

Single-Cycle RISC-V Processor

Submitted in partial fulfilment of the requirements for the award of degree of

Bachelor of Technology

in

Electronics and Communication Engineering

Submitted by:

ROHIL S

PES2UG22EC111

Under the guidance of

Dr Mahesh Awati

Associate Professor

PES University

**DEPARTMENT OF ELECTRONICS AND COMMUNICATION ENGINEERING
PES UNIVERSITY**

(Established under Karnataka Act No. 16 of 2013)

Electronic City, Hosur Road, Bengaluru – 560 100, Karnataka, India

Table of Contents

Sl. No.	Title	Page No.
1	Description	3
2	RTL Code (System Verilog)	3
3	Testbench Code	11
4	Simulation Result	12
5	Schematic	13
6	Applications	13
7	Advantages	13
8	Disadvantages	14
9	Conclusion	14

Description

The **RISC-V processor** is a lightweight, modular, open-source Instruction Set Architecture (ISA) designed for teaching, research, and scalable commercial use. In this project, I implemented a **single-cycle RISC-V processor** using System Verilog, capable of executing basic instructions from the **RV32I** base instruction set.

This processor executes one instruction per clock cycle (single-cycle architecture), and supports:

- **R-type** (e.g. add, sub, and, or)
- **I-type** (e.g. addi, lw)
- **S-type** (e.g. sw)
- **B-type** (e.g. beq)
- **U-type** (e.g. lui)
- **J-type** (e.g. jal)

RTL Code (System Verilog)

```
module riscv_core (  
    input logic clk,  
    input logic reset  
);  
    logic [31:0] pc, next_pc;  
    logic [31:0] instr;  
    logic [4:0] rs1, rs2, rd;  
    logic [31:0] reg_data1, reg_data2, alu_result, imm;  
    logic [31:0] write_data;  
    logic [6:0] opcode;  
    logic [2:0] funct3;  
    logic [6:0] funct7;
```

```

// Fetch
pc_register pc_reg (
    .clk(clk),
    .reset(reset),
    .next_pc(next_pc),
    .pc(pc)
);
instruction_memory imem (
    .addr(pc),
    .instruction(instr)
);

// Decode
assign opcode = instr[6:0];
assign rd     = instr[11:7];
assign funct3 = instr[14:12];
assign rs1    = instr[19:15];
assign rs2    = instr[24:20];
assign funct7 = instr[31:25];

register_file rf (
    .clk(clk),
    .rs1(rs1),
    .rs2(rs2),
    .rd(rd),
    .write_data(write_data),
    .reg_write(reg_write),
    .data1(reg_data1),
    .data2(reg_data2)
);

immediate_generator imm_gen (
    .instr(instr),
    .imm_out(imm)
);

alu alu_unit (

```

```

        .a(reg_data1),
        .b(alu_src ? imm : reg_data2),
        .alu_control(alu_control),
        .result(alu_result)
    );

    data_memory dmem (
        .clk(clk),
        .addr(alu_result),
        .write_data(reg_data2),
        .mem_read(mem_read),
        .mem_write(mem_write),
        .read_data(mem_read_data)
    );

    control_unit control (
        .opcode(opcode),
        .reg_write(reg_write),
        .alu_src(alu_src),
        .mem_to_reg(mem_to_reg),
        .mem_read(mem_read),
        .mem_write(mem_write),
        .alu_op(alu_op),
        .branch(branch)
    );

    alu_control alu_ctrl (
        .alu_op(alu_op),
        .funct3(funct3),
        .funct7(funct7),
        .alu_control(alu_control)
    );

    assign write_data = mem_to_reg ? mem_read_data : alu_result;
    assign next_pc = pc + 4; // Basic PC increment; to be replaced
    with branch logic

```

```
endmodule
```

```
-----  
module pc_register (  
    input logic clk,  
    input logic reset,  
    input logic [31:0] next_pc,  
    output logic [31:0] pc  
);  
    always_ff @(posedge clk or posedge reset) begin  
        if (reset)  
            pc <= 32'h00000000;  
        else  
            pc <= next_pc;  
        end  
endmodule
```

```
-----  
module instruction_memory (  
    input logic [31:0] addr,  
    output logic [31:0] instruction  
);  
    logic [31:0] memory [0:255];  
  
    initial begin  
        // Example: addi x1, x0, 10  
        memory[0] = 32'h00a00093; // addi x1, x0, 10  
        memory[1] = 32'h00100113; // addi x2, x0, 1  
        // Add more instructions here  
    end  
  
    assign instruction = memory[addr[9:2]]; // word aligned  
endmodule
```

```
-----  
module register_file (  
    input logic clk,  
    input logic [4:0] rs1, rs2, rd,  
    input logic [31:0] write_data,  
    input logic reg_write,  
    output logic [31:0] data1, data2
```

```

);
  logic [31:0] registers [0:31];

  always_ff @(posedge clk) begin
    if (reg_write && rd != 0)
      registers[rd] <= write_data;
  end

  assign data1 = registers[rs1];
  assign data2 = registers[rs2];
endmodule

-----

module immediate_generator (
  input  logic [31:0] instr,
  output logic [31:0] imm_out
);
  logic [6:0] opcode;
  assign opcode = instr[6:0];

  always_comb begin
    case (opcode)
      7'b0010011, 7'b0000011: // I-type (addi, lw)
        imm_out = {{20{instr[31]}}, instr[31:20]};
      7'b0100011: // S-type (sw)
        imm_out = {{20{instr[31]}}, instr[31:25], instr[11:7]};
      7'b1100011: // B-type (beq, bne)
        imm_out = {{19{instr[31]}}, instr[31], instr[7],
instr[30:25], instr[11:8], 1'b0};
      7'b0110111: // U-type (lui)
        imm_out = {instr[31:12], 12'b0};
      7'b1101111: // J-type (jal)
        imm_out = {{11{instr[31]}}, instr[31], instr[19:12],
instr[20], instr[30:21], 1'b0};
      default:
        imm_out = 32'd0;
    endcase
  end
endmodule

```

```

module alu (
    input logic [31:0] a, b,
    input logic [3:0] alu_control,
    output logic [31:0] result
);
    always_comb begin
        case (alu_control)
            4'b0000: result = a & b;
            4'b0001: result = a | b;
            4'b0010: result = a + b;
            4'b0110: result = a - b;
            4'b0111: result = (a < b) ? 32'd1 : 32'd0;
            4'b1100: result = a ^ b;
            default: result = 32'd0;
        endcase
    end
endmodule

```

```

module data_memory (
    input logic clk,
    input logic [31:0] addr,
    input logic [31:0] write_data,
    input logic mem_read,
    input logic mem_write,
    output logic [31:0] read_data
);
    logic [31:0] memory [0:255];

    always_ff @(posedge clk) begin
        if (mem_write)
            memory[addr[9:2]] <= write_data;
        end

        assign read_data = mem_read ? memory[addr[9:2]] : 32'd0;
    end
endmodule

```

```

module control_unit (

```



```

input logic [6:0] opcode,
output logic reg_write,
output logic alu_src,
output logic mem_to_reg,
output logic mem_read,
output logic mem_write,
output logic [1:0] alu_op,
output logic branch
);

always_comb begin
  case (opcode)
    7'b0110011: begin // R-type
      alu_src    = 0;
      mem_to_reg = 0;
      reg_write  = 1;
      mem_read   = 0;
      mem_write  = 0;
      branch     = 0;
      alu_op     = 2'b10;
    end
    7'b0010011: begin // I-type (addi)
      alu_src    = 1;
      mem_to_reg = 0;
      reg_write  = 1;
      mem_read   = 0;
      mem_write  = 0;
      branch     = 0;
      alu_op     = 2'b00;
    end
    7'b0000011: begin // Load
      alu_src    = 1;
      mem_to_reg = 1;
      reg_write  = 1;
      mem_read   = 1;
      mem_write  = 0;
      branch     = 0;
      alu_op     = 2'b00;
    end
  end
end

```

```

end
7'b0100011: begin // Store
    alu_src    = 1;
    mem_to_reg = 0; // X
    reg_write  = 0;
    mem_read   = 0;
    mem_write  = 1;
    branch     = 0;
    alu_op     = 2'b00;
end
7'b1100011: begin // Branch
    alu_src    = 0;
    mem_to_reg = 0;
    reg_write  = 0;
    mem_read   = 0;
    mem_write  = 0;
    branch     = 1;
    alu_op     = 2'b01;
end
default: begin
    alu_src    = 0;
    mem_to_reg = 0;
    reg_write  = 0;
    mem_read   = 0;
    mem_write  = 0;
    branch     = 0;
    alu_op     = 2'b00;
end
endcase
end
endmodule

```

```

module alu_control (
    input logic [1:0] alu_op,
    input logic [2:0] funct3,
    input logic [6:0] funct7,
    output logic [3:0] alu_control
);

```

```

always_comb begin
    case (alu_op)
        2'b00: alu_control = 4'b0010; // ADD (lw/sw/addi)
        2'b01: alu_control = 4'b0110; // SUB (branch)
        2'b10: begin // R-type
            case ({funct7, funct3})
                10'b0000000000: alu_control = 4'b0010; // ADD
                10'b0100000000: alu_control = 4'b0110; // SUB
                10'b0000000111: alu_control = 4'b0000; // AND
                10'b0000000110: alu_control = 4'b0001; // OR
                10'b0000000100: alu_control = 4'b1100; // XOR
                default:      alu_control = 4'b1111;
            endcase
        end
        default: alu_control = 4'b0000;
    endcase
end
endmodule

```

Testbench Code

```

`timescale 1ns / 1ps

module tb_riscv_core;
    logic clk;
    logic reset;

    // Instantiate the DUT
    riscv_core uut (
        .clk(clk),
        .reset(reset)
    );

    // Clock generation: 10ns period (100 MHz)
    always #5 clk = ~clk;

```

```

initial begin
    $display("Starting RISC-V Processor Simulation...");

    // Initialize signals
    clk = 0;
    reset = 1;

    // Hold reset for a few cycles
    #20;
    reset = 0;


    // Let the processor run for a while
    #500;

    $display("Simulation Finished.");
    $finish;
end


endmodule





```

Simulation

 

Schematic

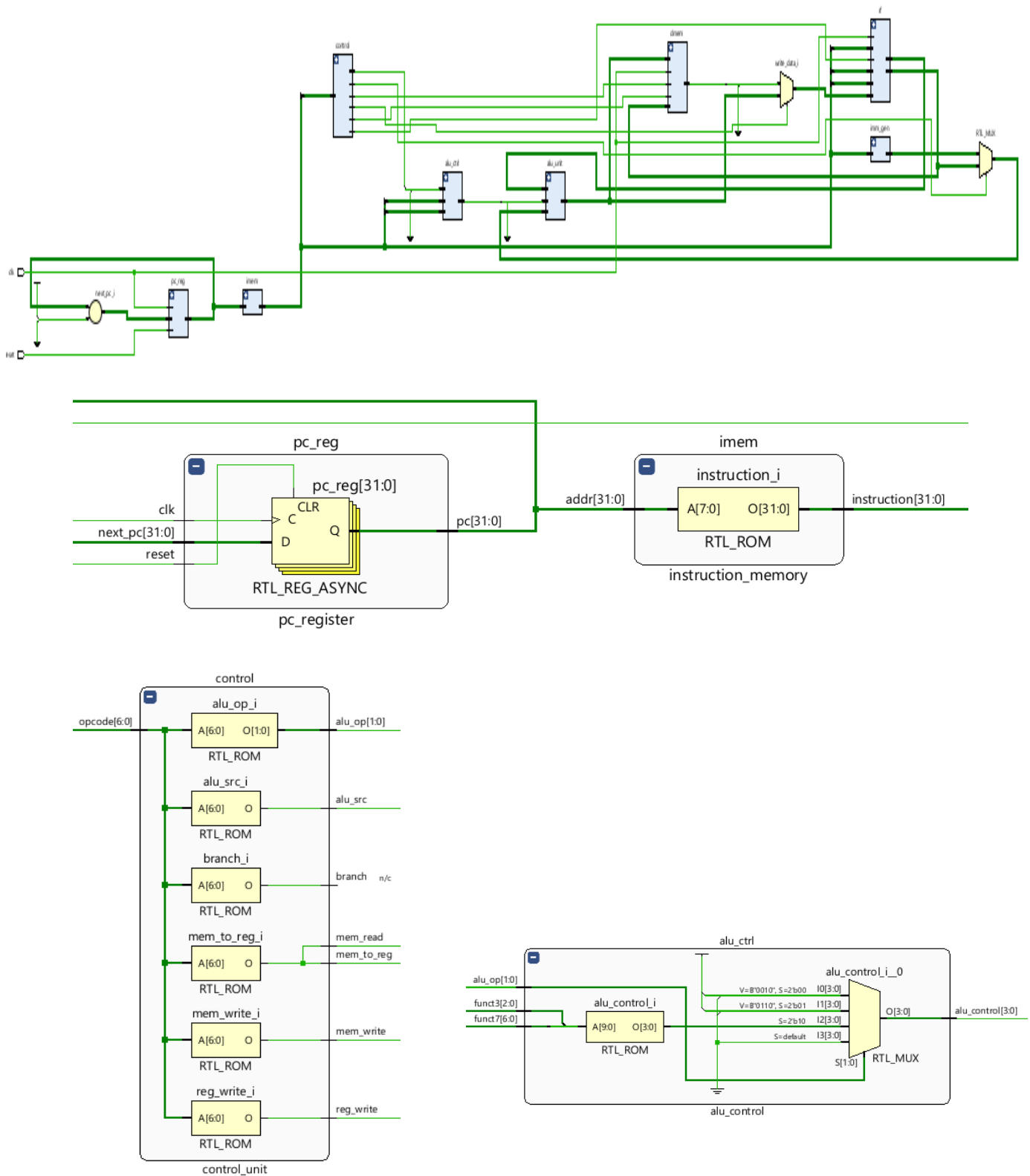

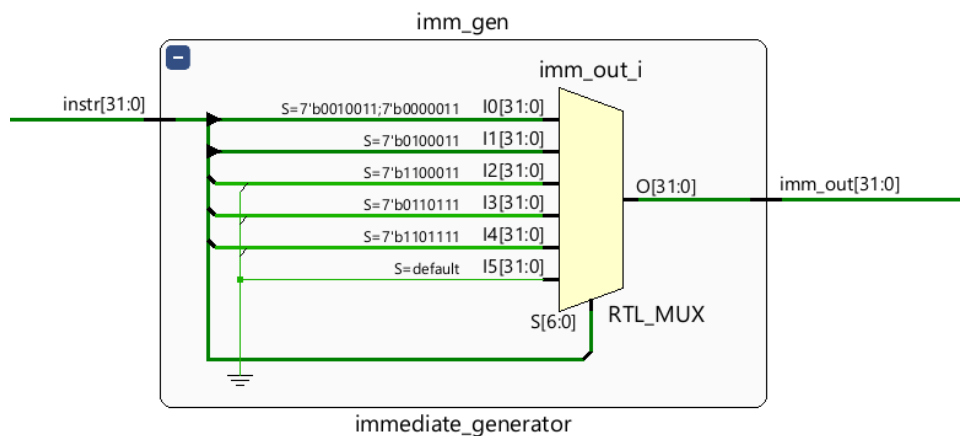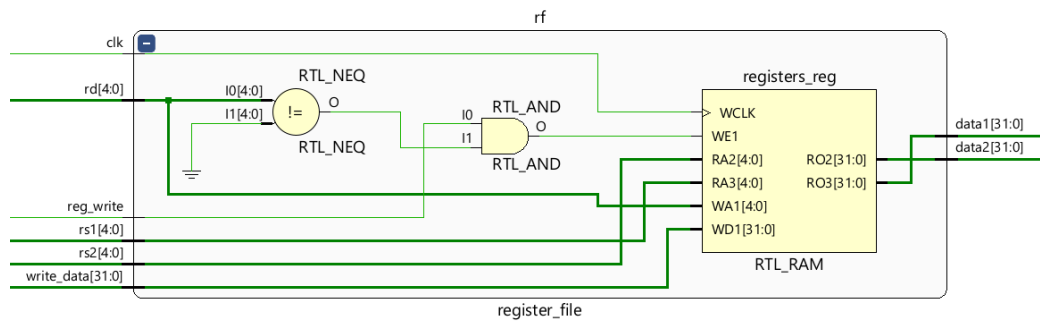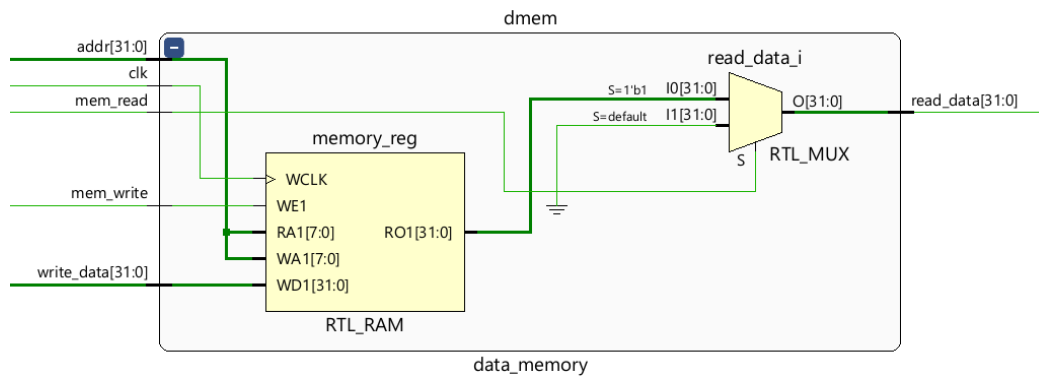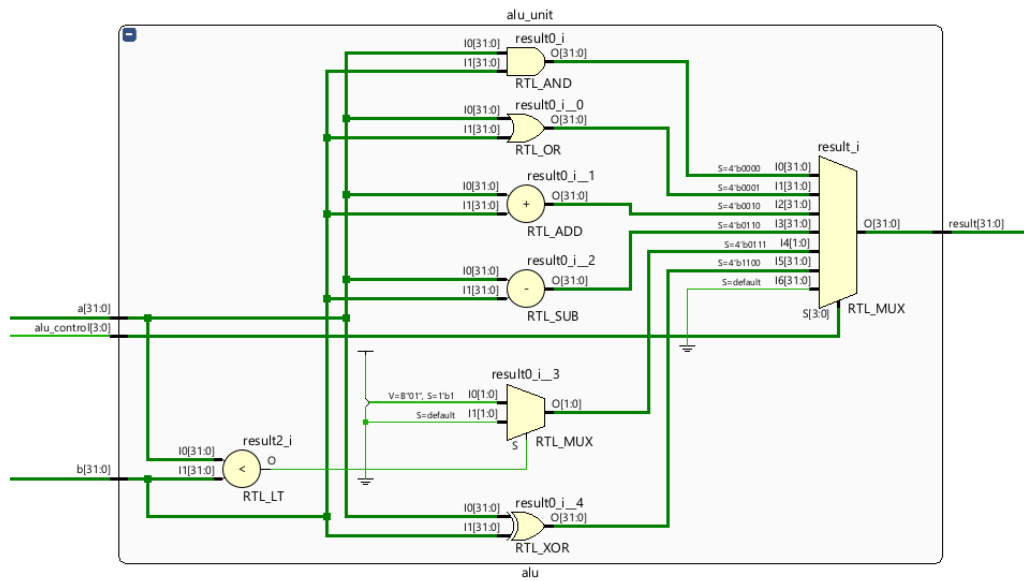

Applications

- Understanding instruction-level execution
- Educational VLSI/FPGA projects
- Foundation for pipelined or multi-cycle CPU design
- Useful in embedded systems with custom ISA extensions

Advantages

- Modular and scalable RTL design
- Fully synthesizable
- Instruction-driven behavior via RISC-V format
- Easily extendable to support more instructions or pipelining

Disadvantages

- No hazard detection (yet)
- Single-cycle limits performance
- No forwarding, pipelining, or branch prediction
- Limited instruction support (subset of RV32I)

Conclusion

Implementing a single-cycle RISC-V processor deepened my understanding of the **hardware-software interface**, **control signals**, and **instruction execution pipelines**. This foundational design sets the stage for adding pipelining, memory-mapped IO, or even custom instructions in the future.